

## LT5 LAPLACE TRANSFORMS – ELECTRICAL CIRCUITS

### Applying Laplace Transforms to Electrical Circuits

#### Example

For the LRC circuit given by

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = E_0 \quad \text{where } \frac{dq}{dt}(0) = q(0) = 0$$

And  $L = 1$ ,  $R = 3$ ,  $C = 0.5$ ,  $E_0 = 10$

Find:

- the charge  $q(t)$  on the capacitor
- the resulting current  $i(t)$  in the circuit, using Laplace transforms

#### Solution

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = E_0$$

Since  $i = \frac{dq}{dt}$  we can write this equation as

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = E_0$$

Since  $L = 1$ ,  $R = 3$ ,  $C = 0.5$ ,  $E_0 = 10$  this equation becomes

$$\frac{d^2q}{dt^2} + 3 \frac{dq}{dt} + 2q = 10$$

Recall that

$$\mathcal{L}\left[\frac{d^2}{dt^2} q(t)\right] = s^2 Q(s) - s \cdot q(0) - q'(0)$$

$$\mathcal{L}\left[\frac{d}{dt} q(t)\right] = sQ(s) - q(0)$$

$$\mathcal{L}[q(t)] = Q(s)$$

$$\mathcal{L}[a] = \frac{a}{s}$$

$$\text{So if } \frac{d^2q}{dt^2} + 3 \frac{dq}{dt} + 2q = 10$$

$$\text{Then } \mathcal{L}\left[\frac{d^2q}{dt^2} + 3 \frac{dq}{dt} + 2q\right] = \mathcal{L}[10]$$

$$\text{And } [s^2 Q(s) - s \cdot q(0) - q'(0)] + 3 [sQ(s) - q(0)] + [2Q(s)] = \frac{10}{s}$$

$$\text{Therefore } s^2 Q(s) + 3sQ(s) + 2Q(s) = \frac{10}{s}$$

And since we are given that  $q(0) = 0$  and  $q'(0) = 0$

$$\Rightarrow Q(s) [s^2 + 3s + 2] = \frac{10}{s}$$

$$\Rightarrow Q(s) = \frac{10}{s[s^2 + 3s + 2]}$$

$$Q(s) = \frac{10}{s(s+1)(s+2)}$$

We can now resolve this into partial fractions

$$\text{Let } \frac{10}{s(s+1)(s+2)} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2}$$

$$\Rightarrow 10 = A(s+1)(s+2) + B(s)(s+2) + C(s)(s+1)$$

$$\text{Setting } s = 0: 10 = 2A \quad \Rightarrow A = 5$$

$$\text{Setting } s = -1: 10 = -B \quad \Rightarrow B = -10$$

$$\text{Setting } s = -2: 10 = 2C \quad \Rightarrow C = 5$$

$$\text{So } Q(s) = \frac{10}{s(s+1)(s+2)}$$

$$\text{Can now be written as: } Q(s) = \frac{5}{s} - \frac{10}{s+1} + \frac{5}{s+2}$$

Now taking the inverse Laplace transform:

$$q(t) = \mathcal{L}^{-1} \left[ \frac{5}{s} - \frac{10}{s+1} + \frac{5}{s+2} \right]$$

$$q(t) = 5 - 10e^{-t} + 5e^{-2t}$$

To find the current  $i(t)$ :

$$i(t) = \frac{dq}{dt} = \frac{d}{dt} (5 - 10e^{-t} + 5e^{-2t}) = 10e^{-t} - 10e^{-2t}$$

Note: This problem could also have been solved using a 2<sup>nd</sup> order differential equation, without Laplace transforms had the question not specifically asked for its solution using Laplace transforms.